
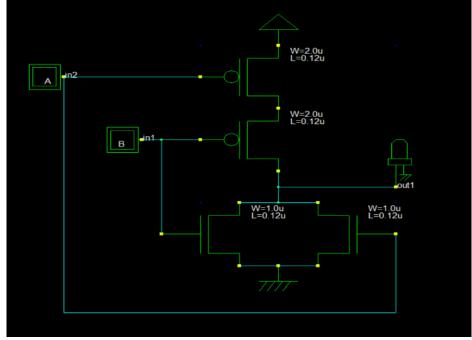



NOT GATE

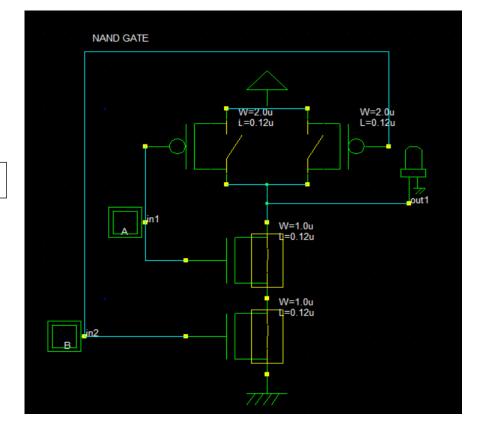


NOR GATE





NAND GATE

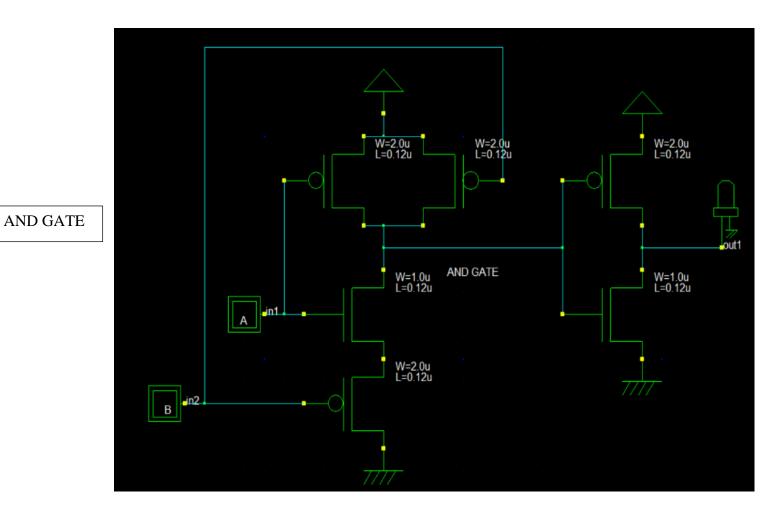


OR GATE

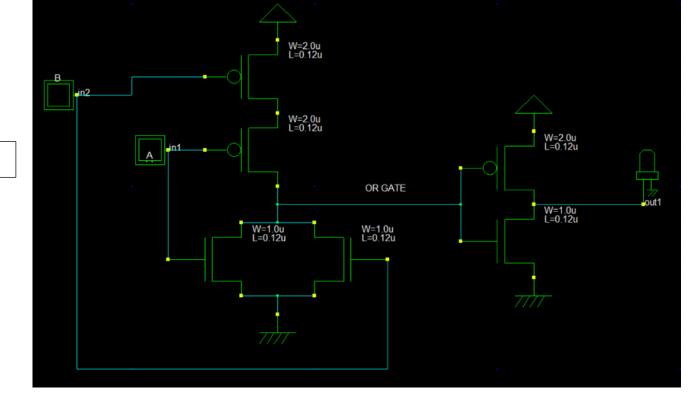

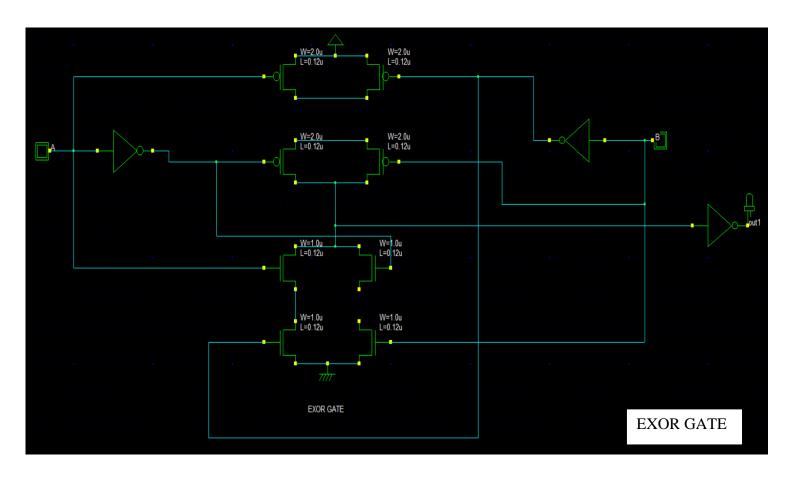

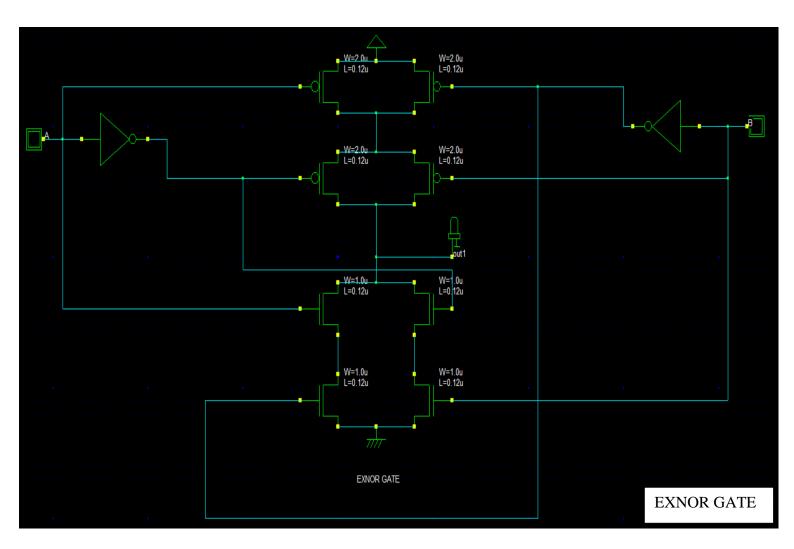

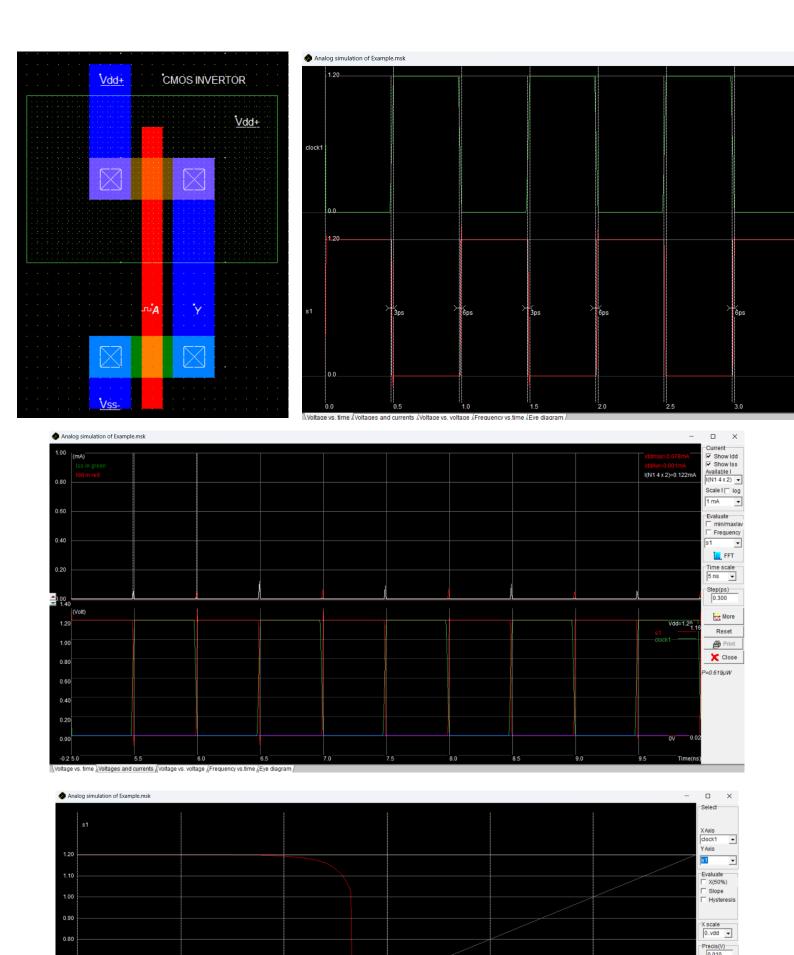

Reset


P=0.619µW

clock1
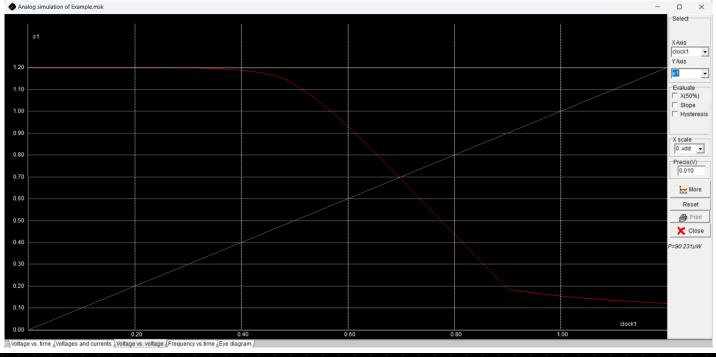
## 1) 7K OHM


Voltage vs. time Voltages and currents (Voltage vs. voltage Frequency vs.time Eye diagram)










## 2) 10K OHM

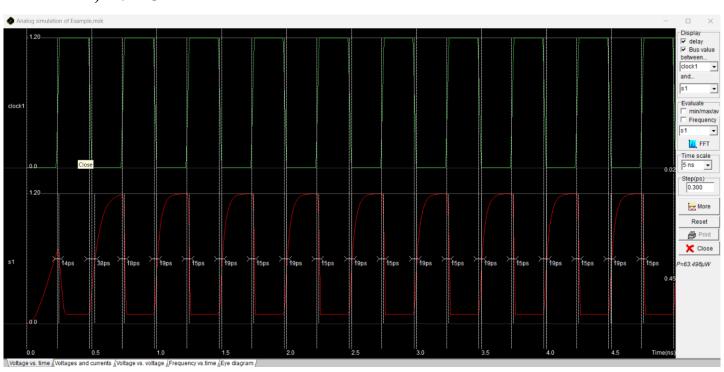


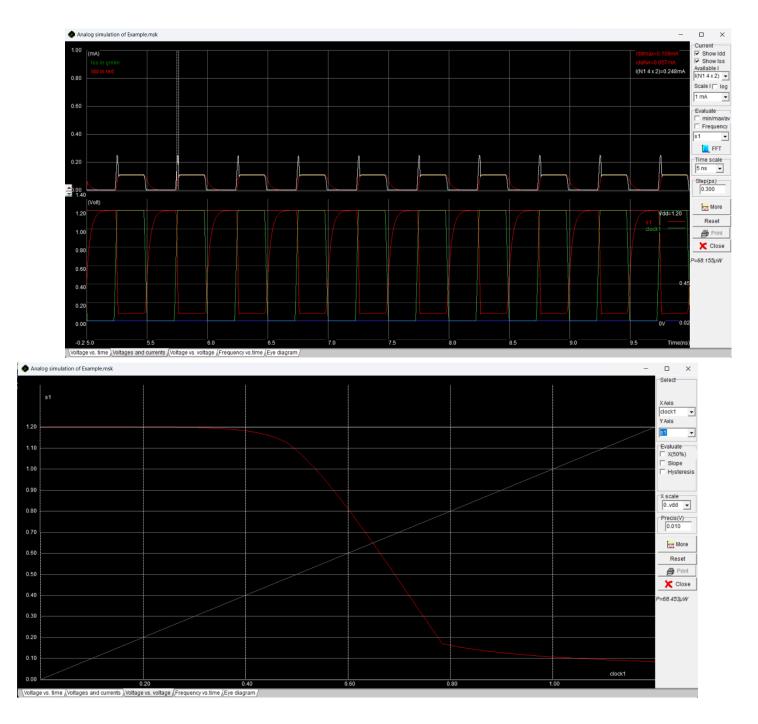


3)17.5K OHM

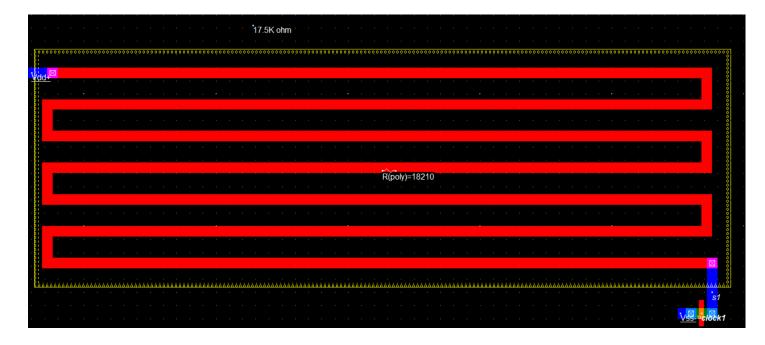


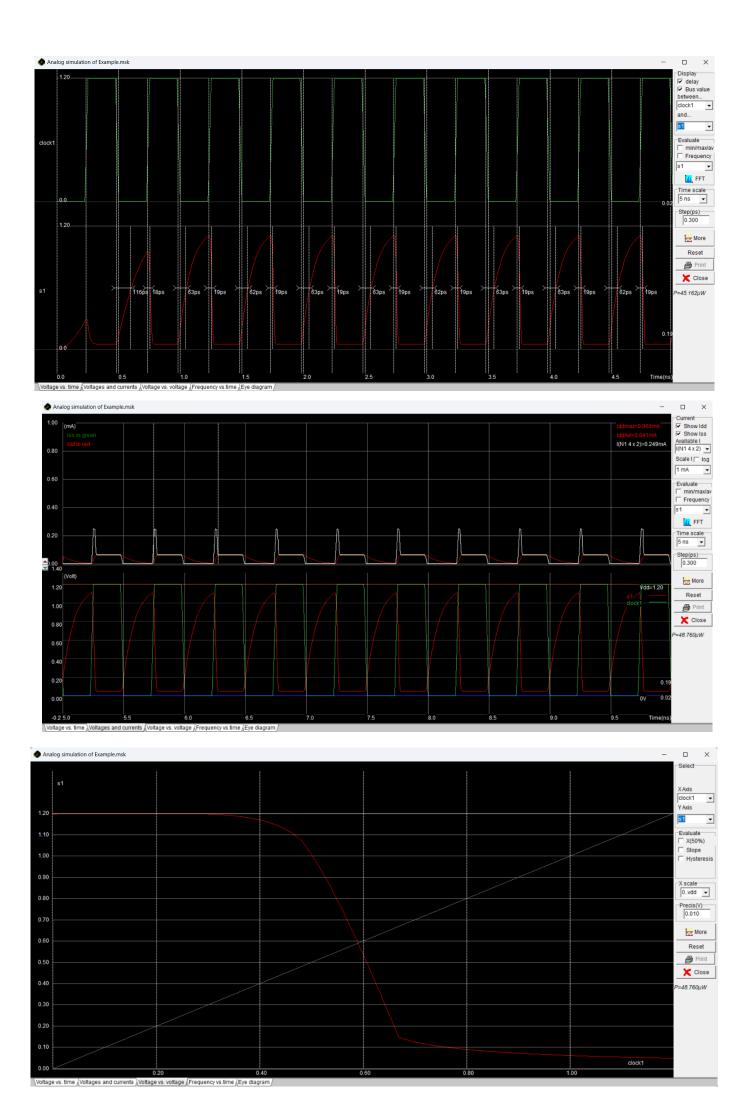

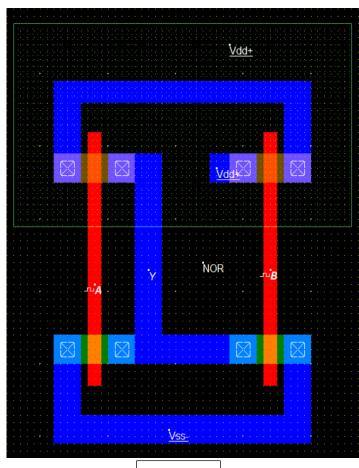

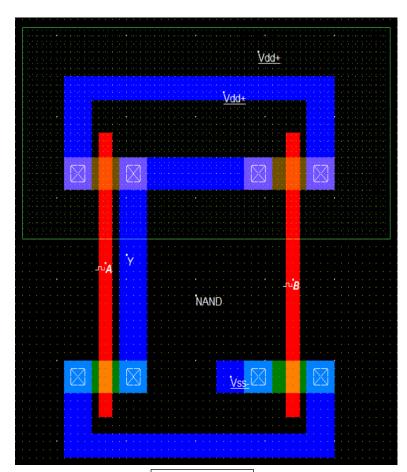

NOR GATE NAND GATE

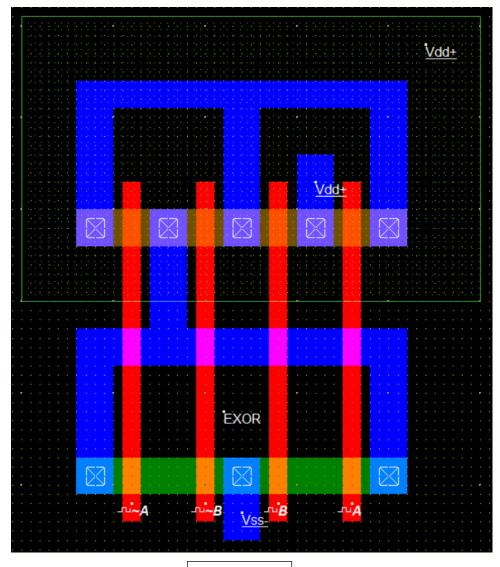

**EXOR GATE**